

LF Network Analyzer

Frank Gentges K0BRA

AMRAD

fgentges@mindspring.com

10/6/02

What and Who Is AMRAD?

- AMRAD is the Amateur Radio Research and Development Corporation
- AMRAD develops technologies for amateur radio and functions much like a radio club
- AMRAD meets once a month locally
- AMRAD meets informally once a week on Saturdays at Tippy's Taco House on Lee Highway at around 12:30


What Is AMRAD Doing for LF

- ✓ FCC has issued an NPRM for amateur LF allocation
- ✓ AMRAD has experimental license for LF
 - ✓ Part 5 license issued by FCC
 - ✓ Single frequency of 136.75 kHz
 - ✓ AMRAD has been operating under this license and learning about LF.
- ✓ AMRAD Developing LF Technology
 - ✓ LF Test Equipment for:
“The Well Equipped LF Laboratory”

LF Current Transformer Design

- Texts generally describe current transformers poorly
 - Assume short circuit across output
 - Neglect magnetizing current
 - Limits wideband use for accurate measurement
 - AMRAD developed more complete understanding of LF current transformer

Current Transformer

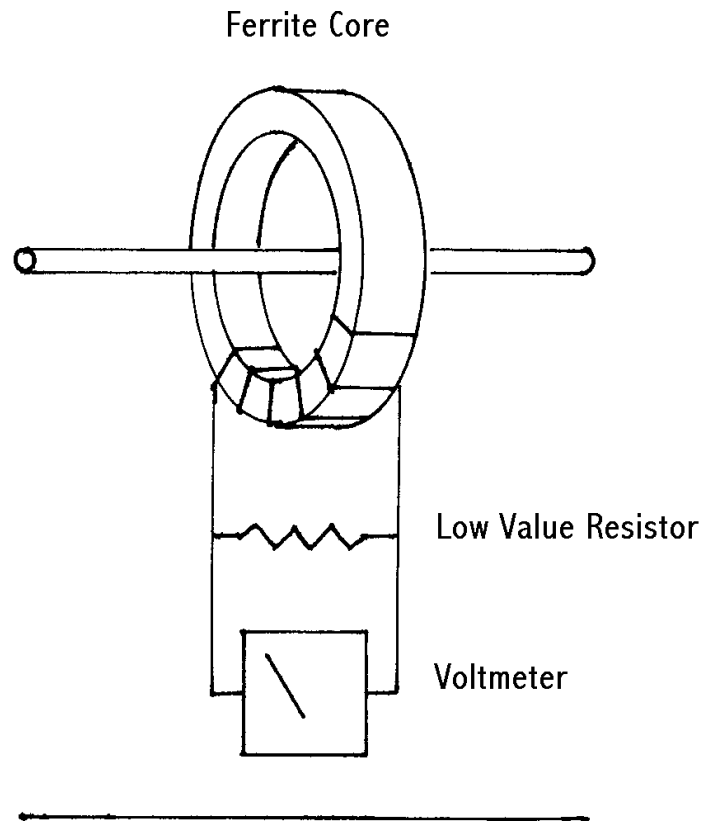

AMRAD Current Transformer Model

- ✓ Accounts for magnetization current
- ✓ Leads to more optimum design
- ✓ Use computer spreadsheet to optimize designs
- ✓ Suggests a simple approach to an impedance meter
 - ✓ Minimize sources of error on spreadsheet

LF Analyzer Concept


- ✓ Use current transformer to read load current
 - ✓ Current is measured as voltage
 - ✓ Phase angle measured between driving voltage and voltage from current transformer
- ✓ Meter reads load impedance magnitude and phase over a wide range
- ✓ Better than classic network analyzer or grid dip meter for the

“Well Equipped LF Laboratory”

LF Analyzer Transformer

- ✓ Use coaxial test lead through core
 - ✓ Test current down center conductor
 - ✓ Confine stray currents back through shield
 - ✓ Current Transformer output magnitude only reflects actual load current
- ✓ Minimize phase shift in transformer
 - ✓ Current transformer output phase accurately reflects voltage and current phase relationship

Network Analyzer Transformer

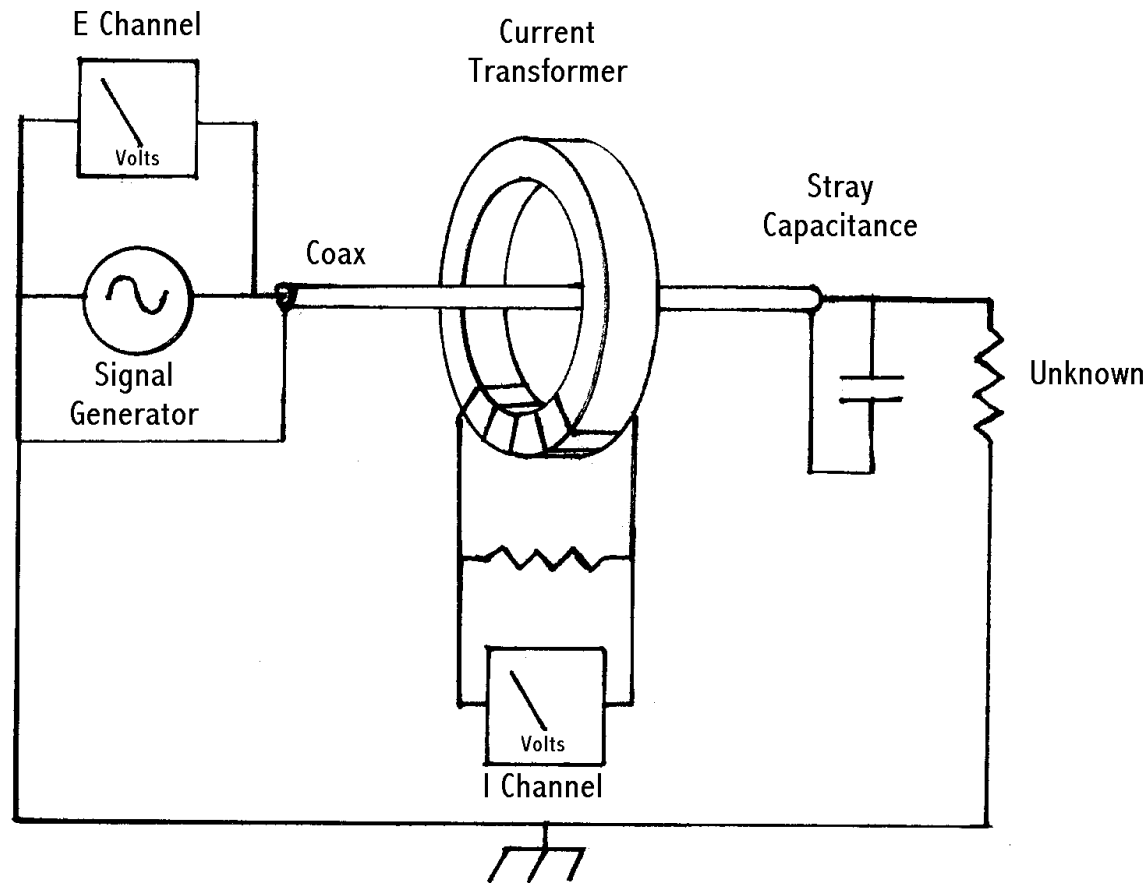

Implementing LF Analyzer

Option 1

- ✓ USE DDS for signal source
- ✓ Use Logamp to measure signal amplitudes
- ✓ Control DDS and read logamp signal with microprocessor

Option 2

- ✓ Use DDS for signal source
- ✓ Use second DDS and DBMs with IF amps and digital attenuators to read signal levels
- ✓ Use microprocessor to control DDSes and attenuators
- ✓ In both cases, use PC to control and report results

LF Analyzer Utility

- ✓ LF Measurement Swiss Army Knife
- ✓ Wider Z range than classic network analyzer
 - ✓ Coil inductance and Q
 - ✓ Antenna impedance before tuning
 - ✓ Quartz crystal impedance
 - ✓ Capacitance
 - ✓ Amplifier input impedance
 - ✓ RF transformer impedance

Initial Tests

- ✓ Current transformer can be made to cover 10 kHz to 16 MHz with low residual errors
- ✓ Inexpensive logamps can cover 60 dB with magnitude errors less than 1 dB
- ✓ LF current transformer design seems to center on 1 amp = 1 volt.
 - Large excursions present too much error
- ✓ Testing with voltmeters on both E and I channels suggests impedance magnitude could be expressed in dB re:1 ohm

Transformer Design

- ✓ FT-50-75 Core, permeability of 5000
- ✓ Primary: 1 turn, brass tubing with coaxial wire
- ✓ Secondary: 25 turns #30 wire wrap wire
- ✓ Secondary termination: 50 ohms
- ✓ Shielding to concentrate stray capacitance to “guard” terminal only

Conclusion

- ✓ LF Network Analyzer based on a wideband current transformer can be made to cover a wide range of impedances
- ✓ Use of DDS and microprocessor control can simplify use, measurements and error corrections
- ✓ Use simple version as VSWR meter alternative